

**Abanob Evram**

**Assignmen1[Extra]**




## [Q1]

### The code:

```
module Q1(A,out);  
    input [3:0] A;  
    output out ;  
    assign out = (2<A&&A<8)?1:0;  
endmodule
```

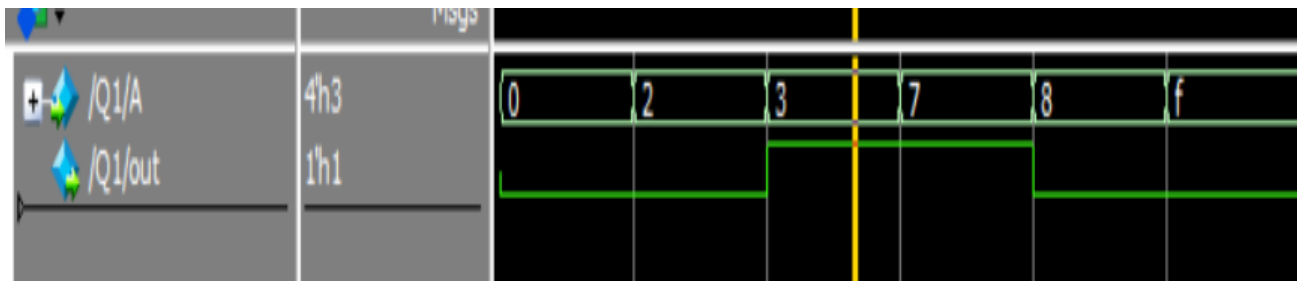1) A four-bit binary number is represented as A3A2A1A0, where A3, A2, A1, and A0 represent the individual bits and A0 is equal to the LSB. Design a logic circuit using Verilog that will produce a HIGH output whenever the binary number is greater than 0010 and less than 1000.

- The design takes 1 input A (4-bits) and output out (1-bit)





[Q2]

2) (a) Draw with your pen on a piece of paper the output waveform F for the circuit of Figure below.

(b) Repeat with the B input held LOW.


(c) Repeat with B held HIGH.

  


**[Q3]** Design the following circuit using Verilog and determine the input conditions needed to produce  $F = 1$

 **The code:**

```
module Q3(A,B,C,F);  
  input A,B,C;  
  output F;  
  wire z0,z1;  
  assign z0 = (A^B) ;  
  assign z1 = ~(B^C);  
  assign F=z0&z1&C;  
endmodule
```



 **Note:** the only case that  $F=1$  it is  $[A=0,B=1,C=1]$



[Q4]


4) Write a Verilog description for a circuit that accepts a three-bit input A and outputs true if the input is a prime number

## The code:

```
module prime(A,Out);
input [2:0] A ;
output reg Out;
always @(*) begin
    case (A)
        2 :Out =1;
        3 :Out =1;
        5 :Out =1;
        7 :Out =1;
        default: Out=0;
    endcase
end
endmodule
```

## Another code:


```
module prime (A,Out);
input [2:0] A;
output Out;
assign out=(A==2 || A==3 || A==5 || A==7)? 1:0;
endmodule
```

 

## [Q5]

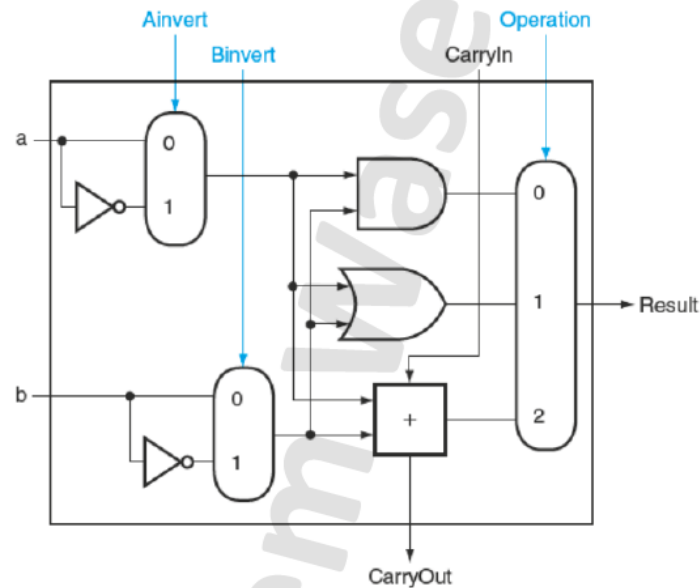5) Implement the following 1-bit ALU. If you are unfamiliar with the concept of an ALU, you can find more information by clicking [here](#). Use conditional operator for the multiplexers. For the 3-to-1 Mux, you can use the following format for the conditional operator.

assign <output\_signal> = <condition1> ? <value1> : <condition2> ? <value2> : <default\_value>;



Port Name	Type	Size	Description
A	Input	1 bit	Input a
B			Input b
<u>Ainvert</u>			Select signal for the multiplexer to select a or a complement
<u>Binvert</u>			Select signal for the multiplexer to select b or b complement
<u>CarryIn</u>			Carry in
Operation	Output	2 bits	Select signal for the multiplexer to drive the Result output
<u>CarryOut</u>		1 bit	Carry out
Result		1 bit	Output of the multiplexer

## The code:

```
module Mux2(In0_Mux2,In1_Mux2,Sel_Mux2,Out_Mux2);  
input In0_Mux2,In1_Mux2,Sel_Mux2;  
output Out_Mux2;  
assign Out_Mux2=(Sel_Mux2==1)?In1_Mux2:In0_Mux2;  
endmodule
```

```
module Mux3(In0_Mux3,In1_Mux3,In2_Mux3,Sel_Mux3,Out_Mux3);  
input In0_Mux3,In1_Mux3,In2_Mux3;  
input [1:0] Sel_Mux3;  
output Out_Mux3;  
assign Out_Mux3=(Sel_Mux3==0)?In0_Mux3:(Sel_Mux3==1)?In1_Mux3:In2_Mux3;  
endmodule
```

```
module Adder2(In0_Adder,In1_Adder,Carryout_Adder,Carryin_Adder,Out_Adder);  
input In0_Adder,In1_Adder,Carryin_Adder;  
output Out_Adder,Carryout_Adder;  
assign Out_Adder =In0_Adder+In1_Adder+Carryin_Adder ;  
assign  
Carryout_Adder=(In0_Adder&In1_Adder)|(Carryin_Adder&In1_Adder)|(Carryin_Adder&In0_Adder);  
endmodule
```

```
module Alu(A,B,Ainvert,Binvert,Carryin,Operation,Carryout,Result);  
input A,B,Ainvert,Binvert,Carryin;  
input [1:0] Operation;  
output Carryout,Result;  
wire Z0,Z1,Z2;  
Mux2 m1(.Sel_Mux2(Ainvert),.In0_Mux2(A),.In1_Mux2(~A),.Out_Mux2(Z0));  
Mux2 m2(.Sel_Mux2(Binvert),.In0_Mux2(B),.In1_Mux2(~B),.Out_Mux2(Z1));
```




Adder2

```
a1(.In0_Adder(Z0),.In1_Adder(Z1),.Carryin_Adder(Carryin),.Carryout_Adder(Carryout),.Out_Adder(Z2));
```

Mux3

```
m3(.Sel_Mux3(Operation),.In0_Mux3(Z0&Z1),.In1_Mux3(Z0|Z1),.In2_Mux3(Z2),.Out_Mux3(Result));
```

endmodule

 

$I_{n0}$	$I_{n1}$	$C_{in}$	out	cout	Full Adder
0	0	0	0	0	
0	0	1	1	0	
0	1	0	1	0	
0	1	1	0	1	
1	0	0	1	0	
1	0	1	0	1	
1	1	0	0	1	
1	1	1	1	1	

$I_{n0} I_{n1}$	00	01	11	10
$C_{in}$	0	0	1	0
1	0	1	1	1

$C_{out} = I_{n0} I_{n1} + I_{n0} C_{in} + I_{n1} C_{in}$