

Combinational Circuit Design

Design the following circuits with Verilog using assign statements.


1) A four-bit binary number is represented as A3A2A1A0, where A3, A2, A1, and A0 represent the individual bits and A0 is equal to the LSB. Design a logic circuit using Verilog that will produce a HIGH output whenever the binary number is greater than 0010 and less than 1000.

- The design takes 1 input **A** (4-bits) and output **out** (1-bit)


2) (a) Draw with your pen on a piece of paper the output waveform F for the circuit of Figure below.

(b) Repeat with the B input held LOW.

(c) Repeat with B held HIGH.

 

 
3) Design the following circuit using Verilog and determine the input conditions needed to produce $F = 1$



4) Write a Verilog description for a circuit that accepts a three-bit input A and outputs true if the input is a prime number

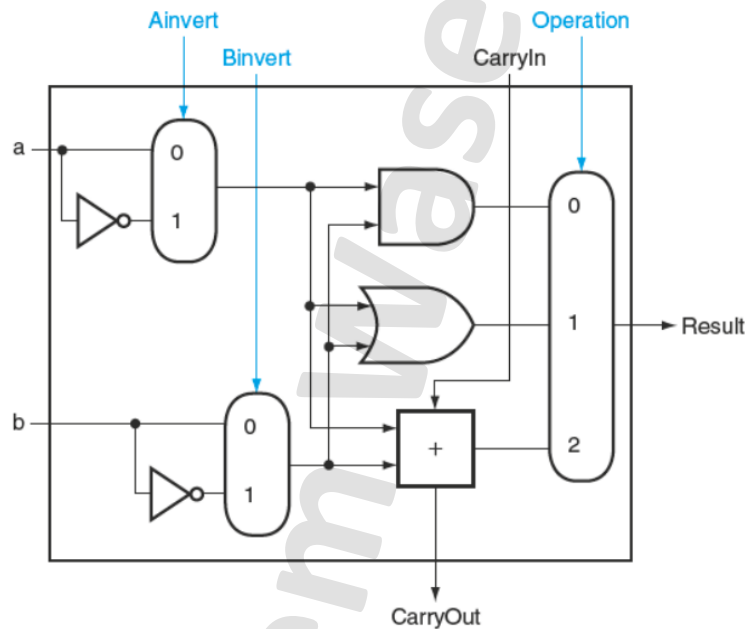5) Implement the following 1-bit ALU. If you are unfamiliar with the concept of an ALU, you can find more information by clicking [here](#). Use conditional operator for the multiplexers. For the 3-to-1 Mux, you can use the following format for the conditional operator.

assign <output_signal> = <condition1> ? <value1> : <condition2> ? <value2> : <default_value>;



Port Name	Type	Size	Description
A	Input	1 bit	Input a
B			Input b
<u>Ainvert</u>			Select signal for the multiplexer to select a or a complement
<u>Binvert</u>			Select signal for the multiplexer to select b or b complement
<u>CarryIn</u>			Carry in
Operation	Output	2 bits	Select signal for the multiplexer to drive the Result output
<u>CarryOut</u>		1 bit	Carry out
Result		1 bit	Output of the multiplexer

Deliverables: The assignment should be submitted as a PDF file with this format <your_name>_Assignment1_extended for example Kareem_Waseem_Assignment1_extended.

Note that your document should be organized as 5 sections corresponding to each design above, and in each section, I am expecting the Verilog code for the design, and waveform snippets forcing different input values to verify the functionality of the design.