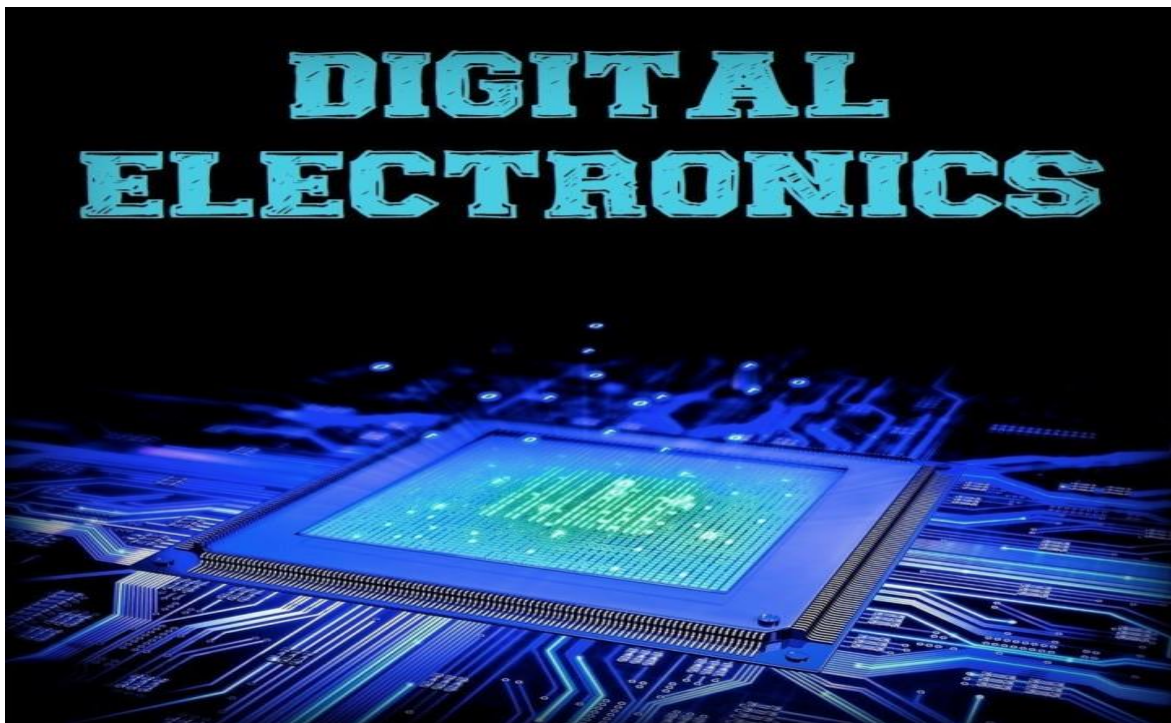


Abanob Evram

Assignmen2



- The design has 5 inputs and 2 outputs
- Randomize the stimulus in the testbench and make sure that the output is correct from the waveform


[Q1]

The design code:

```

module Q1(D,A,B,C,Sel,Out,Out_bar);
input [2:0] D;
input A,B,C,Sel ;
output Out,Out_bar;
wire Z0,Z1,Z2;
assign Z0=D[0]&D[1];
assign Z1=Z0|D[2];
assign Z2=~(A^B^C);
assign Out=(Sel==1)?Z2:Z1;
assign Out_bar=~(Out);
endmodule

```

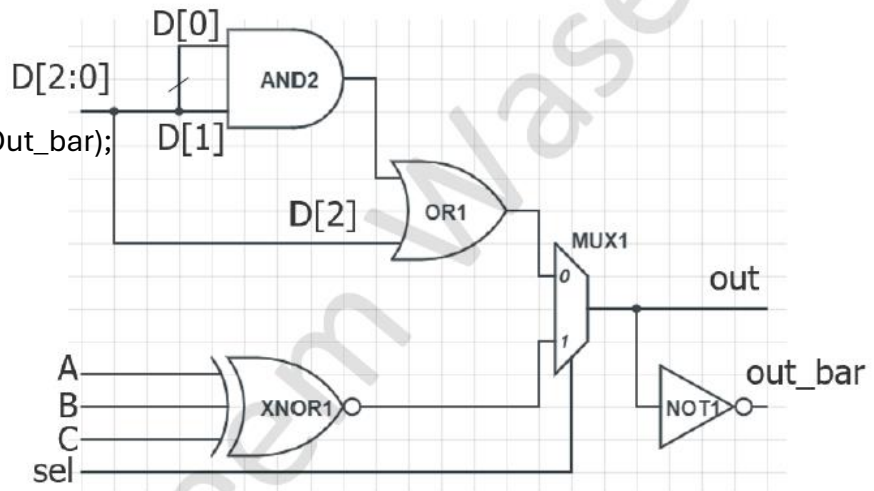

The testbench code:

```


module Q1_tb_randomized();
reg [2:0] D_tb;
reg A_tb,B_tb,C_tb,Sel_tb,Out_expected,Out_bar_expected;
wire Out_dut,Out_bar_dut;
Q1 Dut(D_tb,A_tb,B_tb,C_tb,Sel_tb,Out_dut,Out_bar_dut);
integer i ;
initial begin
    for (i=0;i<99;i=i+1)begin
        A_tb=$random;
        B_tb=$random;
        C_tb=$random;
        D_tb=$random;
        Sel_tb=$random;
        Out_expected=(Sel_tb==1)?(~(A_tb^B_tb^C_tb)):((D_tb[0]&D_tb[1])|(D_tb[2]));
        Out_bar_expected =~(Out_expected);
        #10
        if(Out_expected!=Out_dut)begin
            $display("Error...");
            $stop;
        end
    end
end

```

```

$stop;
end
initial begin
$monitor("Out_expected =%d , Out_dut=%d",Out_expected,Out_dut);
end
endmodule

```

 

[Q2] 2) Design a 4-bit priority encoder, the following truth table is provided where x is 4-bit input and y is a 2-bit output. Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.

The design code:

```
module Priority_encoder(X,Y);
input [3:0] X;
output reg [1:0] Y ;
always @(*) begin
if (X[3]==1)
Y=3;
else if (X[2]==1)
Y=2;
else if (X[1]==1)
Y=1;
else
Y=0;
end
endmodule
```

x3	x2	x1	x0	y1	y0
1	X	X	X	1	1
0	1	X	X	1	0
0	0	1	X	0	1
0	0	0	X	0	0

The testbench code:

```
module Priority_encoder_tb();
reg [3:0] X_tb;
reg [1:0] Y_expected;
wire [1:0] Y_dut;
Priority_encoder dut(X_tb,Y_dut);
integer i;
initial begin
for(i=0;i<99;i=i+1)begin
X_tb=$random;
casex(X_tb)
'b1xxx:Y_expected=3;
'b01xx:Y_expected=2;
'b001x:Y_expected=1;
'b000x:Y_expected=0;
endcase
#10
if(Y_expected!=Y_dut)begin
$display("Error...");
$stop;
end
end
```

```

        end
$stop;
end
initial begin
$monitor ("Y_excpeted=%d , Y_dut=%d",Y_excpeted,Y_dut);
end
endmodule

```

Note: I do not need to use else or default because I wrote all cases

		0101	1010	0101	0111	0010	1111	0010	1110	1000	0101	1100	1101		0101	0011	1010	0000		1010
/Priority_encoder_t...	4b1110	2	3	2		1	3	1	3		2	3			2	1	3	0		3
/Priority_encoder_t...	2h3	2	3	2		1	3	1	3		2	3			2	1	3	0		3
/Priority_encoder_t...	2h3	2	3	2		1	3	1	3		2	3			2	1	3	0		3
/Priority_encoder_tbj	32'd23	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31	32	33	34

		1100	1010	1011	0001	0101	1111	1011	1010	1110	0101	0001	1001	0010	1100	1111		1000	0111	1111
/Priority_encoder_t...	4b0000	3			0	2	3				2	0	3	1	3				2	3
/Priority_encoder_t...	2h0	3			0	2	3				2	0	3	1	3				2	3
/Priority_encoder_t...	2h0	3			0	2	3				2	0	3	1	3				2	3
/Priority_encoder_tbj	32'd83	60	61	62	63	64	65	66	67	68	69	70	71	72	73	74	75	76	77	78

[Q3]

The design code:

```
module BCD(D,Y);
input [9:0] D;
output reg [3:0] Y;
always @(*) begin
    case(D)
        2:Y=1;
        4:Y=2;
        8:Y=3;
        16:Y=4;
        32:Y=5;
        64:Y=6;
        128:Y=7;
        256:Y=8;
        512:Y=9;
        default: Y=0;
    endcase
end
endmodule
```

3) Design a decimal to BCD "Binary Coded Decimal" encoder has 10 input lines D0 to D9 and 4 output lines Y0 to Y3 . Below is the truth table for a decimal to BCD encoder. Output should be held LOW if none of the following input patterns is observed. Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.

Input										Output			
D ₉	D ₈	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

The testbench code:

```
module BCD_tb();
reg [9:0] D_tb;
reg [3:0] Y_expected;
wire [3:0] Y_dut;
BCD dut(D_tb,Y_dut);
integer i;
initial begin
    for(i=0;i<1000;i=i+1)begin
        D_tb=$random;
        if (D_tb==2)Y_expected=1;
        else if(D_tb==4)Y_expected=2;
        else if(D_tb==8)Y_expected=3;
        else if(D_tb==16)Y_expected=4;
        else if(D_tb==32)Y_expected=5;
        else if(D_tb==64)Y_expected=6;
        else if(D_tb==128)Y_expected=7;
    end
end
```

```

else if(D_tb==256)Y_expected=8;
else if(D_tb==512)Y_expected=9;
else Y_expected=0;
#10
if (Y_expected!=Y_dut) begin
$display("ERROR...");
$stop;
end

        end
$stop;
end
initial begin
$monitor("Y_expected=%d , Y_dut=%d , iteration=%d",Y_expected,Y_dut,i);
end
endmodule

```

D_tb	10'h124	124	281	209	263	30d	18d	065	212	301	10d
Y_expected	4'h0	0									
Y_dut	4'h0	0									
i	32'h00000000	00000000	00000001	00000002	00000003	00000004	00000005	00000006	00000007	00000008	00000009
D_tb	10'h124	124	281	209	263	30d	18d	065	212	301	10d
Y_expected	4'h0	0									
Y_dut	4'h0	0									
i	32'd0	0	1	2	3	4	5	6	7	8	9

4) Implement N-bit adder using Dataflow modeling style

[Q4]

The design code:

```
module N_bit_Adder(A,B,C);
parameter N = 1;
input [N-1:0] A,B;
output [N-1:0] C ;
assign C = A+B;
endmodule
```

The testbench code:

```
module N_bit_Adder_tb();
parameter N_tb =4 ;
reg [N_tb-1:0] A_tb,B_tb,C_expected;
wire[N_tb-1:0] C_dut;
N_bit_Adder #(N_tb) dut(A_tb,B_tb,C_dut);
integer i ;
initial begin
    for(i=0;i<99;i=i+1)begin
        A_tb=$random;
        B_tb=$random;
        C_expected=A_tb+B_tb;
        #10
        if(C_dut!=C_expected)begin
            $display("Error...");
            $stop;
        end
    end
    $stop;
end
initial begin
    $monitor("A_tb=%d , B_tb=%d , C_expected=%d ,iteration=%d",A_tb,B_tb,C_expected,i);
end
endmodule
```

A_tb	4'd4	4	9	13	5	1	6	13	9	5		2
B_tb	4'd1	1	3	13	2	13		12	6	10	7	15
C_expected	4'd5	5	12	10	7	14	3	9	15		12	1
C_dut	4'd5	5	12	10	7	14	3	9	15		12	1
i	32'd0	0	1	2	3	4	5	6	7	8	9	10

5) Design N-bit ALU that perform the following operations


[Q5]

The design code:

```
module N_bit_Adder(A,B,C);
parameter N = 1;
input [N-1:0] A,B;
output [N-1:0] C ;
assign C = A+B;
endmodule
```

- The design has 3 inputs and 1 output
- Instantiate the half adder from the previous design to implement the addition operation of the ALU
- For the subtraction, subtract B from A "A - B"
- Parameter N has default value = 4.
- Randomize the stimulus in the testbench and add an expected result y in your testbench code and make the testbench self-checking.

Inputs		Outputs
opcode		Operation
0	0	Addition
1	0	Subtraction
0	1	OR
1	1	XOR

 

A diagram of a diagram
Description automa

```
module N_bit_Alu(A,B,Opcode,Result);
parameter N = 4 ;
input [N-1:0] A,B;
input [1:0] Opcode ;
output reg [N-1:0] Result ;
wire [N-1:0] Adder_result ;
N_bit_Adder #(N) m1(A,B,Adder_result);
always @(*) begin
    if (Opcode==0)
        Result=Adder_result;
    else if (Opcode==1)
        Result=A|B;
    else if (Opcode==2)
        Result=A-B;
    else if (Opcode==3)
        Result=A^B;
end
endmodule
```

The testbench code:

```
module N_bit_Alu_tb();
parameter N_tb =4;
reg [N_tb-1:0] A_tb,B_tb,Result_expected;
reg [1:0] Opcode_tb;
wire [N_tb-1:0] Result_dut;
N_bit_Alu #(N_tb) dut(A_tb,B_tb,Opcode_tb,Result_dut);
integer i ;
initial begin
    for(i=0;i<99;i=i+1)begin
```

```

A_tb=$random;
B_tb=$random;
Opcode_tb=$random;
    case(Opcode_tb)
0:Result_expected=A_tb+B_tb;
1:Result_expected=A_tb|B_tb;
2:Result_expected=A_tb-B_tb;
3:Result_expected=A_tb^B_tb;
endcase
#10
if(Result_expected!=Result_dut)begin
$display ("Error...");
$stop;
end
end
$stop;
end
initial begin
$monitor("A_tb=%d , B_tb=%d , Opcode_tb=%d ,
Result_expected=%d",A_tb,B_tb,Opcode_tb,Result_expected);
end
endmodule

```

A_tb	4'b1000	0100	0011	0101	1101		0110	0101	1111	1000	1101	0011	0000	0110	0011	0010	1111	1010
B_tb	4'b0101	0001	1101	0010	0110	1100	0101	0111	0010	0101	1101	1010		0011	1011	1110	0011	1100
Result_expected	4'b1101	0101	1111	0111	1111	1101	0001	1110	1101				1010	0111	1011	1110	1100	1110
Opcode_tb	2'd0	1				2			0	1	0	1				2		
Result_dut	4'b1101	0101	1111	0111	1111	1101	0001	1110	1101				1010	0111	1011	1110	1100	1110
i	32'd8	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16



A_tb	4'b1001	1001	0111	1100	0111	1110	1111	1000	1111	0110	1010	0011	1111	1011	1001	0101	1001	1010
B_tb	4'b1101	1001	0001	0010	1101		0011	1011	1010	1110	0110	1111	0100	0110	1101	0101	0100	1011
Result_expected	4'b1100	0010	0110	1110	1010	1111		1011	1001	0100	1100		1011	0101	1100	0000	1101	1111
Opcode_tb	2'd2	0	2	0	2	1		0		3			2		3	0	2	
Result_dut	4'b1100	0010	0110	1110	1010	1111		1011	1001	0100	1100		1011	0101	1100	0000	1101	1111
i	32'd40	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43

[Q6]

6) Implement 4-bit ALU display on 7 Segment LED Display

- The design has 4 inputs: A, B, opcode, enable.
- The design has 7 outputs (a-g)
- Instantiate the N-bit ALU designed in the previous design with parameter N = 4
- ALU should execute the operation on A and B depending on the input opcode
- ALU output should be considered as the digit to be displayed on the 7 segment LED display
- Below the truth table of the 7-segment decoder
- Since we have verified the ALU and Adder, we need to make sure that the outputs a to g are correct. Write 16 directed test vectors to exercise all the below digits with enable input equals to 1 then one directed test vector to drive the enable to 0. Make the testbench self-checking.

	Input		Output						
Digit	enable	a	b	c	d	e	f	g	
0	1	1	1	1	1	1	1	0	
1	1	0	1	1	0	0	0	0	
2	1	1	1	0	1	1	0	1	
3	1	1	1	1	1	0	0	1	
4	1	0	1	1	0	0	1	1	
5	1	1	0	1	1	0	1	1	
6	1	1	0	1	1	1	1	1	
7	1	1	1	1	0	0	0	0	
8	1	1	1	1	1	1	1	1	
9	1	1	1	1	1	0	1	1	
A	1	1	1	1	0	1	1	1	
b	1	0	0	1	1	1	1	1	
C	1	1	0	0	1	1	1	0	
d	1	0	1	1	1	1	0	1	
E	1	1	0	0	1	1	1	1	
F	1	1	0	0	0	1	1	1	
x	0	0	0	0	0	0	0	0	

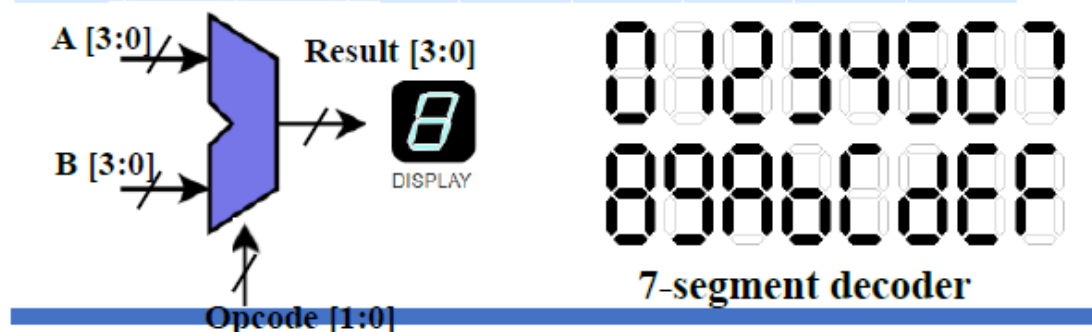 

The design code:

```
module N_bit_Adder(A,B,C);
parameter N = 1;
input [N-1:0] A,B;
output [N-1:0] C ;
assign C = A+B;
endmodule
```

```
module N_bit_Alu(A,B,Opcode,Result);
parameter N = 4 ;
input [N-1:0] A,B;
input [1:0] Opcode ;
output reg [N-1:0] Result ;
wire [N-1:0] Adder_result ;
N_bit_Adder #(N) m1(A,B,Adder_result);
always @(*) begin
    if (Opcode==0)
        Result=Adder_result;
    else if (Opcode==1)
        Result=A|B;
    else if (Opcode==2)
        Result=A-B;
    else if (Opcode==3)
        Result=A^B;
end
endmodule
```

```
module SSD(A,B,Opcode,Enable,a,b,c,d,e,f,g);
parameter N_SSD = 4;
input [N_SSD-1:0] A,B;
input [1:0] Opcode;
input Enable ;
output reg a,b,c,d,e,f,g;
wire [N_SSD-1:0] Result_alu;
N_bit_Alu #(N_SSD) Alu(A,B,Opcode,Result_alu);
always @(*) begin
    case({Result_alu,Enable})
        5'b00001:{a,b,c,d,e,f,g}=7'b1111110;//0
        5'b00011:{a,b,c,d,e,f,g}=7'b0110000;//1
```

```

5'b00101:{a,b,c,d,e,f,g}=7'b1101101;//2
5'b00111:{a,b,c,d,e,f,g}=7'b1111001;//3
5'b01001:{a,b,c,d,e,f,g}=7'b0110011;//4
5'b01011:{a,b,c,d,e,f,g}=7'b1011011;//5
5'b01101:{a,b,c,d,e,f,g}=7'b1011111;//6
5'b01111:{a,b,c,d,e,f,g}=7'b1110000;//7
5'b10001:{a,b,c,d,e,f,g}=7'b1111111;//8
5'b10011:{a,b,c,d,e,f,g}=7'b1111011;//9
5'b10101:{a,b,c,d,e,f,g}=7'b1110111;//a
5'b10111:{a,b,c,d,e,f,g}=7'b0011111;//b
5'b11001:{a,b,c,d,e,f,g}=7'b1001110;//c
5'b11011:{a,b,c,d,e,f,g}=7'b0111101;//d
5'b11101:{a,b,c,d,e,f,g}=7'b1001111;//e
5'b11111:{a,b,c,d,e,f,g}=7'b1000111;//f
default : {a,b,c,d,e,f,g}=0;
endcase
end
endmodule

```

The testbench code:

```


module SSD_tb();
parameter N_SSD_tb = 4;
reg [N_SSD_tb-1:0] A_tb,B_tb;
reg [1:0] Opcode_tb;
reg Enable_tb,a,b,c,d,e,f,g; //a:g expected
wire a_dut,b_dut,c_dut,d_dut,e_dut,f_dut,g_dut;
SSD #(N_SSD_tb) S0(A_tb,B_tb,Opcode_tb,Enable_tb,
a_dut,b_dut,c_dut,d_dut,e_dut,f_dut,g_dut);
//Note OP=0:ADD,OP=1:OR,OP=2:SUB,OP=3:XOR
initial begin
#0 A_tb=10;B_tb=10;Opcode_tb=2;Enable_tb=1;{a,b,c,d,e,f,g}=7'b1111110;//0
#10 A_tb=1;B_tb=0;Opcode_tb=1;Enable_tb=1;{a,b,c,d,e,f,g}=7'b0110000;//1
#10 A_tb=10;B_tb=8;Opcode_tb=3;Enable_tb=1;{a,b,c,d,e,f,g}=7'b1101101;//2
#10 A_tb=1;B_tb=2;Opcode_tb=0;Enable_tb=1;{a,b,c,d,e,f,g}=7'b1111001;//3
#10 A_tb=2;B_tb=2;Opcode_tb=0;Enable_tb=1;{a,b,c,d,e,f,g}=7'b0110011;//4
#10 A_tb=7;B_tb=2;Opcode_tb=2;Enable_tb=1;{a,b,c,d,e,f,g}=7'b1011011;//5
#10 A_tb=8;B_tb=2;Opcode_tb=2;Enable_tb=1;{a,b,c,d,e,f,g}=7'b1011111;//6
#10 A_tb=5;B_tb=2;Opcode_tb=1;Enable_tb=1;{a,b,c,d,e,f,g}=7'b1110000;//7
#10 A_tb=15;B_tb=7;Opcode_tb=3;Enable_tb=1;{a,b,c,d,e,f,g}=7'b1111111;//8

```

```

#10 A_tb=4;B_tb=5;Opcode_tb=0;Enable_tb=1;{a,b,c,d,e,f,g}=7'b11110111;//9
#10 A_tb=5;B_tb=5;Opcode_tb=0;Enable_tb=1;{a,b,c,d,e,f,g}=7'b11101111;//a
#10 A_tb=12;B_tb=1;Opcode_tb=2;Enable_tb=1;{a,b,c,d,e,f,g}=7'b00111111;//b
#10 A_tb=15;B_tb=3;Opcode_tb=2;Enable_tb=1;{a,b,c,d,e,f,g}=7'b10011110;//c
#10 A_tb=5;B_tb=8;Opcode_tb=1;Enable_tb=1;{a,b,c,d,e,f,g}=7'b01111011;//d
#10 A_tb=7;B_tb=7;Opcode_tb=0;Enable_tb=1;{a,b,c,d,e,f,g}=7'b10011111;//e
#10 A_tb=15;B_tb=0;Opcode_tb=2;Enable_tb=1;{a,b,c,d,e,f,g}=7'b10001111;//f
#10 A_tb=5;B_tb=5;Opcode_tb=0;Enable_tb=0;{a,b,c,d,e,f,g}=0;
#10
if({a_dut,b_dut,c_dut,d_dut,e_dut,f_dut,g_dut}!={a,b,c,d,e,f,g})begin
$display("Errrrror...");
$stop;
end
$stop;
end
initial begin
$monitor("A_tb=%d,B_tb=%d,Opcode_tb=%d,Enable_tb=%d,{a,b,c,d,e,f,g}=%b",
        A_tb,B_tb,Opcode_tb,Enable_tb,{a,b,c,d,e,f,g});
end
endmodule

```

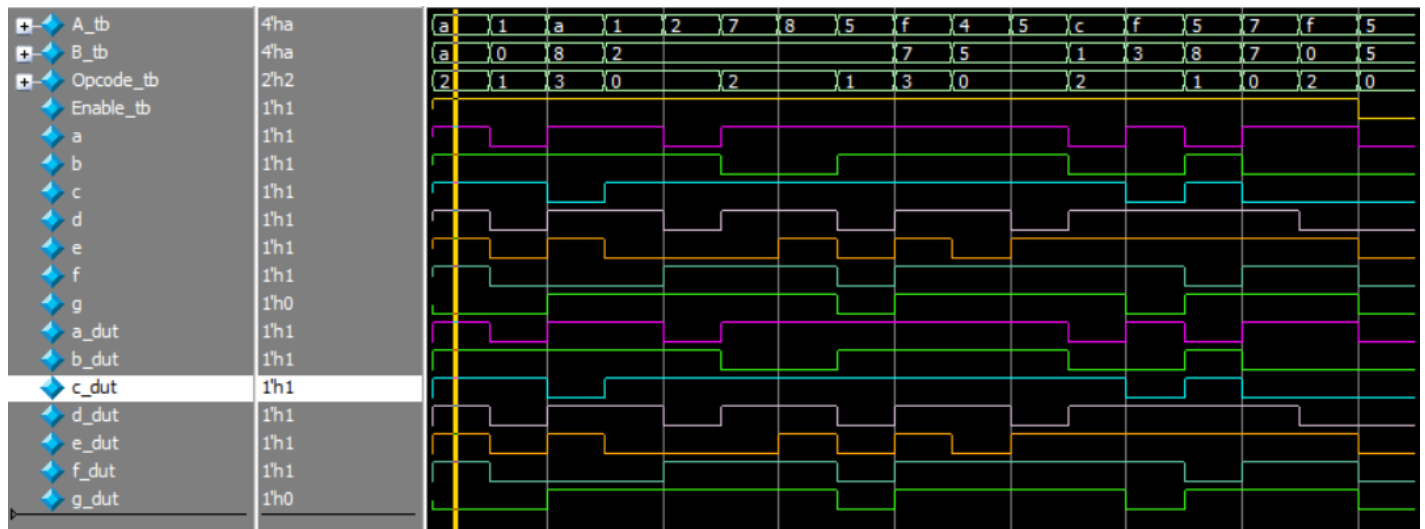

```

# A_tb=10,B_tb=10,Opcode_tb=2,Enable_tb=1,{a,b,c,d,e,f,g}=1111110
# A_tb= 1,B_tb= 0,Opcode_tb=1,Enable_tb=1,{a,b,c,d,e,f,g}=0110000
# A_tb=10,B_tb= 8,Opcode_tb=3,Enable_tb=1,{a,b,c,d,e,f,g}=1101101
# A_tb= 1,B_tb= 2,Opcode_tb=0,Enable_tb=1,{a,b,c,d,e,f,g}=1111001
# A_tb= 2,B_tb= 2,Opcode_tb=0,Enable_tb=1,{a,b,c,d,e,f,g}=0110011
# A_tb= 7,B_tb= 2,Opcode_tb=2,Enable_tb=1,{a,b,c,d,e,f,g}=1011011
# A_tb= 8,B_tb= 2,Opcode_tb=2,Enable_tb=1,{a,b,c,d,e,f,g}=1011111
# A_tb= 5,B_tb= 2,Opcode_tb=1,Enable_tb=1,{a,b,c,d,e,f,g}=1110000
# A_tb=15,B_tb= 7,Opcode_tb=3,Enable_tb=1,{a,b,c,d,e,f,g}=1111111
# A_tb= 4,B_tb= 5,Opcode_tb=0,Enable_tb=1,{a,b,c,d,e,f,g}=1111011
# A_tb= 5,B_tb= 5,Opcode_tb=0,Enable_tb=1,{a,b,c,d,e,f,g}=1110111
# A_tb=12,B_tb= 1,Opcode_tb=2,Enable_tb=1,{a,b,c,d,e,f,g}=0011111
# A_tb=15,B_tb= 3,Opcode_tb=2,Enable_tb=1,{a,b,c,d,e,f,g}=1001110
# A_tb= 5,B_tb= 8,Opcode_tb=1,Enable_tb=1,{a,b,c,d,e,f,g}=0111101
# A_tb= 7,B_tb= 7,Opcode_tb=0,Enable_tb=1,{a,b,c,d,e,f,g}=1001111
# A_tb=15,B_tb= 0,Opcode_tb=2,Enable_tb=1,{a,b,c,d,e,f,g}=1000111
# A_tb= 5,B_tb= 5,Opcode_tb=0,Enable_tb=0,{a,b,c,d,e,f,g}=0000000

```