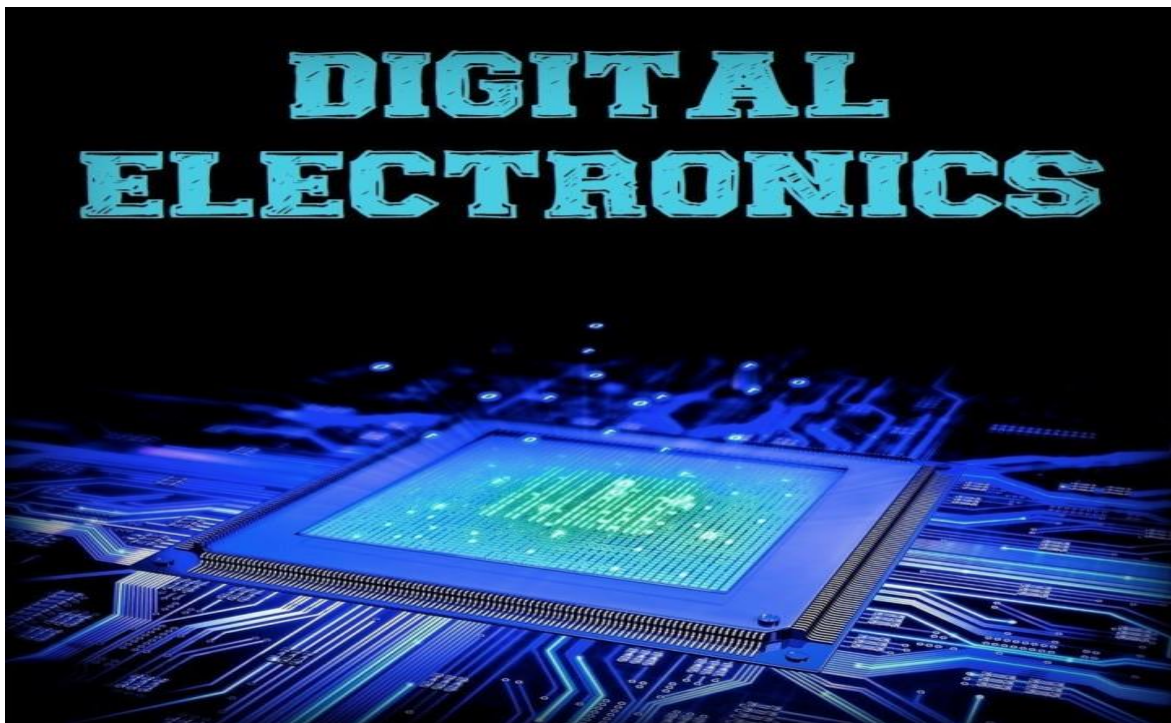


Abanob Evram

Assignmen3



[Q1]

The design code:

```
module latch(aset,data,gate,aclr,q);
parameter LAT_WIDTH=6;
input aset,gate,aclr;
input [LAT_WIDTH-1:0] data;
output reg [LAT_WIDTH-1:0] q;
always @(*) begin
    if(aclr)
        q<=0;
    else if (aset)
        q<={LAT_WIDTH{1'b1}};
    else if (gate)
        q<=data;
    end
endmodule
```

The testbench code:

```
module latch_tb();
parameter LATCH_WIDTH_tb = 6;
reg aset_tb,gate_tb,aclr_tb;
reg [LATCH_WIDTH_tb-1:0] data_tb,q_expected;
wire [LATCH_WIDTH_tb-1:0] q_dut;
latch #(LATCH_WIDTH_tb) dut(aset_tb,data_tb,gate_tb,aclr_tb,q_dut);
integer i;
initial begin
    aset_tb=0;aclr_tb=1;data_tb=0;gate_tb=0;q_expected=0;
    if(q_dut!=q_expected) begin
        $display("errorr");
        $stop;
    end
    #10
    for (i=0;i<99;i=i+1) begin
        aset_tb=$random;
        aclr_tb=$random;
        gate_tb=$random;
        data_tb=$random;
```

1) Implement the following latch as specified below

Parameters

LAT_WIDTH: Determine the width of input data and output q


Ports

Name	Type	Description
aset	Input	Asynchronous set input. Sets q[] output to 1.
data[]		Data Input to the D-type latch with width LAT_WIDTH
gate		Latch enable input
aclr		Asynchronous clear input. Sets q[] output to 0.
q[]	Output	Data output from the latch with with LAT_WIDTH

```

if(aclr_tb)
    q_expected<=0;
else if (aset_tb)
    q_expected<={LATCH_WIDTH_tb{1'b1}};
else if (gate_tb)
    q_expected<=data_tb;
#10
if(q_expected!=q_dut)begin
    $display("Errorr");
    $stop;
end
end
$stop;
end
endmodule

```

 

[Q2]

```
module reg_blocking1(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

always @(posedge clk) begin
    if (rst) begin
        q1 = 0;
        q2 = 0;
        out = 0;
    end
    else begin
        q1 = in;
        q2 = q1;
        out = q2;
    end
end
endmodule
```

```
module reg_non_blocking1(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

always @(posedge clk) begin
    if (rst) begin
        q1 <= 0;
        q2 <= 0;
        out <= 0;
    end
    else begin
        q1 <= in;
        q2 <= q1;
        out <= q2;
    end
end
endmodule
```

```
module reg_blocking2(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

always @(posedge clk) begin
    if (rst) begin
        q2 = 0;
        q1 = 0;
        out = 0;
    end
    else begin
        q2 = q1;
        q1 = in;
        out = q2;
    end
end
endmodule
```

```
module reg_non_blocking2(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

always @(posedge clk) begin
    if (rst) begin
        q2 <= 0;
        q1 <= 0;
        out <= 0;
    end
    else begin
        q2 <= q1;
        q1 <= in;
        out <= q2;
    end
end
endmodule
```

```
module reg_blocking3(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

always @(posedge clk) begin
    if (rst) begin
        out = 0;
        q2 = 0;
        q1 = 0;
    end
    else begin
        out = q2;
        q2 = q1;
        q1 = in;
    end
end
endmodule
```

```
module reg_non_blocking3(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

always @(posedge clk) begin
    if (rst) begin
        out <= 0;
        q2 <= 0;
        q1 <= 0;
    end
    else begin
        out <= q2;
        q2 <= q1;
        q1 <= in;
    end
end
endmodule
```

2-

```
module comb_blocking1(clk, a, b, c, y);
input a, b, c, clk;
output reg y;

reg x;

always @(posedge clk) begin
    x = a & b;
    y = x | c;
end

endmodule
```

```
module comb_non_blocking1(clk, a, b, c, y);
input a, b, c, clk;
output reg y;

reg x;

always @(posedge clk) begin
    x <= a & b;
    y <= x | c;
end

endmodule
```

```
module comb_blocking2(clk, a, b, c, y);
input a, b, c, clk;
output reg y;

reg x;

always @(posedge clk) begin
    y = x | c;
    x = a & b;
end

endmodule
```

```
module comb_non_blocking2(clk, a, b, c, y);
input a, b, c, clk;
output reg y;

reg x;

always @(posedge clk) begin
    y <= x | c;
    x <= a & b;
end

endmodule
```

```
module comb_non_blocking3(clk, a, b, c, y);
input a, b, c, clk;
output reg y;

reg x;
reg y_comb;

always @(*) begin
    x = a & b;
    y_comb = x | c;
end


always @(posedge clk) begin
    y <= y_comb;
end

endmodule
```



*

[2]


1- reg_blocking1

  reg_non_blocking1 // reg_non_blocking2
reg_non_blocking3 // reg_blocking3


rst




2- reg_blocking2

 

2- Comb_blocking1 // Comb_non_blocking2

 

 Comb_non_blocking1 // Comb_blocking2 // Comb_non_blocking3



[Q3]

The design code:

```
module Counter(clk,set,out);
input clk,set;
output reg [3:0] out;
always @(posedge clk or negedge set) begin
    if(~set)
        out<=4'b1111;
    else
        out<=out+1;
end
endmodule
```

The testbench code:

```
module Counter_golden_tb();
reg clk,set;
wire [3:0] out_behavioral,out_structural;
Ripple_counter golden(clk,set,out_structural);
Counter dut(clk,set,out_behavioral);
initial begin
    clk=0;
    forever
        #1 clk=~clk;
    end
integer i;
initial begin
    set=0;
    @(negedge clk);
    if(out_behavioral!=out_structural)begin
        $display("Errrrrr");
        $stop;
    end
    set=1;
    for(i=0;i<50;i=i+1)begin
        @(negedge clk);
        if(out_behavioral!=out_structural)begin
            $display("Errrrrr");
            $stop;
        end
    end
end
```

3)

1. Implement 4-bit counter with asynchronous active low set using behavioral modelling that increment from 0 to 15

• Input:

- clk
- set (sets all bits to 1)
- out (4-bits)

2. Use the structural counter done in Assignment3_v13 as a golden reference.

3. Test the above behavioral design using a self-checking testbench

— Testbench should instantiate both structural and behavioral counters.

```

        end
    end
    $stop;
end
endmodule

```

The do file code:

```
vlib work
```


```
vlog D_Flipflop.v Ripple_counter.v Counte.v Counte_tb.v
```

```
vsim -voptargs=+acc Counter_golden_tb
```

```
add wave *
```

```
run -all
```

```
#quit -sim
```

 

[Q4]

- 4) Extend on the previous counter done in question 3 to have extra 2 single bit outputs (div_2 and div_4). Hint: Observe the output bits of the "out" bus to generate the following
- div_2: output signal that acts as output clock with a frequency half the input clock signal.
 - div_4: output signal that acts as output clock with a frequency quarter the input clock signal.

The design code:

```
module Extend_counter(clk,set,out,div_2,div_4);
input clk,set;
output reg [3:0] out ;
output div_2,div_4;
always @(posedge clk or negedge set) begin
    if(~set)
        out<=4'b1111;
    else
        out<=out+1;
    end
assign div_2 = out[0];
assign div_4 = out[1];
endmodule
```

The testbench code:

```
module Extend_counter_tb();
reg clk,set;
wire [3:0] out_extend,out_structural;
wire div_2_extend,div_4_extend,div_2_structural,div_4_structural;
Ripple_counter golden(clk,set,out_structural);
Extend_counter dut(clk,set,out_extend,div_2_extend,div_4_extend);
assign div_2_structural = out_structural[0];
assign div_4_structural = out_structural[1];
initial begin
    clk=0;
    forever
        #1 clk=~clk;
end
integer i;
initial begin
    set=0;
    @(negedge clk);
    if(out_extend!=out_structural) $display("Errrrrr in output");
    if(div_2_extend!=div_2_structural) $display("Errrrrr in div_2");
    if(div_4_extend!=div_4_structural) $display("Errrrrr in div_4");
    set=1;
end
```

```

for (i=0;i<50;i=i+1) begin
    @(negedge clk);
    if(out_extend!=out_structural) $display("Errrrrr in output");
    if(div_2_extend!=div_2_structural) $display("Errrrrr in div_2");
    if(div_4_extend!=div_4_structural) $display("Errrrrr in div_4");
end
$stop;
end
endmodule

```

