

Assignment 4 Extra

Design the following circuits using Verilog and create a testbench for each design to check its functionality. Create a do file for question 1.

1)

1. Implement 4-bit Ripple counter with asynchronous active low set using behavioral modelling that increment from 0 to 15

- Input:
 - clk
 - set (sets all bits to 1)
 - out (4-bits)

2. Use the structural counter done in the previous assignment as a golden reference.

3. Test the above behavioral design using a self-checking testbench


— Testbench should instantiate the previous two designs

2) Extend on the previous counter done in the previous question to have extra 2 single bit outputs (div_2 and div_4). Hint: Observe the output bits of the “out” bus to generate the following

- div_2: output signal that divides the input clock by 2
- div_4: output signal that divides the input clock by 4

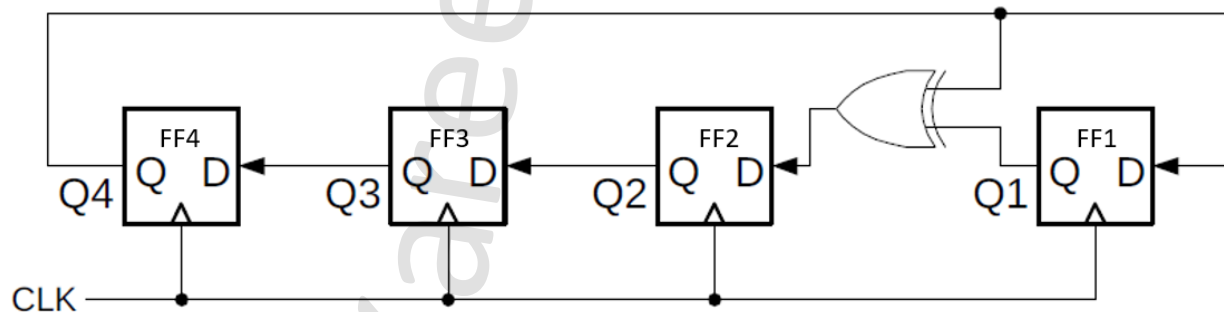3) Implement the following Linear feedback shift register (LFSR)

- LFSR Inputs: clk, rst, set
- LFSR output: out (4 bits) where out[3] is connected to Q4, out[2] is connected to Q3, etc.



- LFSR can be used as a random number generator.
- The sequence is a random sequence where numbers appear in a random sequence and repeats as shown on the figure on the right

FF2, FF3, FF4 have the following specifications:

- D input
- Clk input
- Input async rst (active high) – resets output to 0
- Output Q

FF1 have the following specifications:

- D input
- Clk input
- Input async set (active high) – set output to 1
- Output Q

Note: the rst and set signals should be activated at the same time to guarantee correct operation

0001
0010
0100
1000
0011
0110
1100
1011
0101
1010
0111
1110
1111
1101
1001
0001



4) Implement N-bit parameterized Full/Half adder

- Parameters
 - WIDTH: Determine the width of input a,b, sum
 - PIPELINE_ENABLE: if this parameter is high then the output of the sum and carry will be available in the positive clock edge (sequential) otherwise the circuit is pure combinational, default is high. Valid values: 0 or 1.
 - USE_FULL_ADDER: if this parameter is high then cin signal will be used during the cout and sum calculation from the input signals, otherwise if this parameter is low ignore the cin input, default is high
- Ports

Name	Type	Description
a	Input	Data input a of width determined by WIDTH parameter
b		Data input b of width determined by WIDTH parameter
clk		Clk input
cin		Carry in bit
rst	Output	Active high synchronous reset
sum		sum of a and b input of width determined by WIDTH parameter
cout		Carry out bit

5) Implement shift register with the following specs:

Parameter:

1. SHIFT_DIRECTION: specify shifting direction either LEFT or RIGHT, default = "LEFT"
2. SHIFT_AMOUNT: specify the number of bits to be shifted, possible values are 1, 2, 3, 4, 5, 6, 7. Default = 1

Ports:

1. Inputs:
 - clk
 - rst (async active high)
 - load: control signal if high, register should be loaded with the input "load_value"
 - load_value: value to be loaded to the register
2. Outputs:
 - PO (8 bits): parallel out which represent the register to be shifted.

Create 2 testbench to test the operation of the register when shifting right and shift amount is 2 and the other testbench to test the shifting left and shift amount is 1. The following specs should be tested:

1. Test reset that it forces the output to zero
2. Load signal to load a randomized value to the output
3. Test the shifting operation on the output
4. Load another randomized value to the output
5. Test the shifting again

Use Questasim waveform to check the above functionality

6) Implement a gray counter

Inputs:

- clk
- rst

Outputs:

- gray_out, 2-bit output

Hint: create a 2-bit binary counter counting 0, 1, 2, 3 and use the relation between the binary counter and the gray counter to assign the output bits. The most significant bit will be the same while the least significant bit of the gray out will be the reduction xor of the binary counter bits.

Create a testbench testing the following:

1. rst to force output to zero

2. remove reset and check the gray pattern from the waveform

Deliverables:

- 1) The assignment should be submitted as a PDF file with this format <your_name>_Assignment4 for example Kareem_Waseem_Assignment4
- 2) Snippets from the waveforms captured from QuestaSim for each design with inputs assigned values and output values visible.

Note that your document should be organized as 6 sections corresponding to each design above, and in each section, I am expecting the Verilog code, and the waveforms snippets